

# CHAPTER HEADINGS

## PREFACE & ACKNOWLEDGEMENTS

| CHAPTER  | PAGE |
|--|------|
| <b>PART 1: THE RADIO VALVE</b>                                     |      |
| 1 INTRODUCTION TO THE RADIO VALVE                                  | 1    |
| 2 VALVE CHARACTERISTICS  | 13   |
| 3 THE TESTING OF OXIDE-COATED CATHODE HIGH-VACUUM RECEIVING VALVES | 68   |
| <b>PART 2: GENERAL THEORY AND COMPONENTS</b>                       |      |
| 4 THEORY OF NETWORKS   | 128  |
| 5 TRANSFORMERS AND IRON-CORED INDUCTORS                            | 199  |
| 6 MATHEMATICS  | 254  |
| 7 NEGATIVE FEEDBACK  | 306  |
| 8 WAVE MOTION AND THE THEORY OF MODULATION                         | 403  |
| 9 TUNED CIRCUITS   | 407  |
| 10 CALCULATION OF INDUCTANCE                                       | 429  |
| 11 DESIGN OF RADIO FREQUENCY INDUCTORS                             | 450  |
| <b>PART 3: AUDIO FREQUENCIES</b>                                   |      |
| 12 AUDIO FREQUENCY VOLTAGE AMPLIFIERS                              | 481  |
| 13 AUDIO FREQUENCY POWER AMPLIFIERS                                | 544  |
| 14 FIDELITY AND DISTORTION   | 603  |
| 15 TONE COMPENSATION AND TONE CONTROL                              | 635  |
| 16 VOLUME EXPANSION, COMPRESSION AND LIMITING                      | 679  |
| 17 REPRODUCTION FROM RECORDS                                       | 701  |
| 18 MICROPHONES, PRE-AMPLIFIERS, ATTENUATORS AND MIXERS             | 775  |
| 19 UNITS FOR THE MEASUREMENT OF GAIN AND NOISE                     | 806  |
| 20 LOUDSPEAKERS  | 831  |
| 21 THE NETWORK BETWEEN THE POWER OUTPUT STAGE AND THE LOUDSPEAKER  | 880  |
| <b>PART 4: RADIO FREQUENCIES</b>                                   |      |
| 22 AERIALS AND TRANSMISSION LINES                                  | 890  |
| 23 RADIO FREQUENCY AMPLIFIERS                                      | 912  |
| 24 OSCILLATORS   | 947  |
| 25 FREQUENCY CONVERSION AND TRACKING                               | 962  |
| 26 INTERMEDIATE FREQUENCY AMPLIFIERS                               | 1020 |
| 27 DETECTION AND AUTOMATIC VOLUME CONTROL                          | 1072 |
| 28 REFLEX AMPLIFIERS   | 1140 |
| 29 LIMITERS AND AUTOMATIC FREQUENCY CONTROL                        | 1147 |
| <b>PART 5: RECTIFICATION, REGULATION, FILTERING AND HUM</b>        |      |
| 30 RECTIFICATION   | 1161 |
| 31 FILTERING AND HUM   | 1192 |
| 32 VIBRATOR POWER SUPPLIES   | 1202 |
| 33 CURRENT AND VOLTAGE REGULATORS                                  | 1213 |
| <b>PART 6: COMPLETE RECEIVERS</b>                                  |      |
| 34 TYPES OF A-M RECEIVERS  | 1223 |
| 35 DESIGN OF SUPERHETERODYNE A-M RECEIVERS                         | 1228 |
| 36 DESIGN OF F-M RECEIVERS   | 1287 |
| 37 RECEIVER AND AMPLIFIER TESTS AND MEASUREMENTS                   | 1297 |
| <b>PART 7: SUNDRY DATA</b>   |      |
| 38 TABLES, CHARTS AND SUNDRY DATA                                  | 1328 |
| See next page for detailed List of Contents.                       |      |
| SUPPLEMENT   | 1475 |
| INDEX  | 1433 |

# CONTENTS

## PART 1 : THE RADIO VALVE

| SECTION  | PAGE |
|--|------|
| <b>CHAPTER 1. INTRODUCTION TO THE RADIO VALVE</b>      |      |
| 1. ELECTRICITY AND EMISSION                            | 1    |
| 2. THE COMPONENT PARTS OF RADIO VALVES                 | 4    |
| (i) Filaments, cathodes and heaters                    | 4    |
| (ii) Grids   | 5    |
| (iii) Plates   | 5    |
| (iv) Bulbs   | 5    |
| (v) Voltages with valve operation                      | 5    |
| 3. TYPES OF RADIO VALVES                               | 6    |
| (i) Diodes   | 6    |
| (ii) Triodes   | 7    |
| (iii) Tetrodes   | 7    |
| (iv) Pentodes  | 7    |
| (v) Pentode power amplifiers                           | 8    |
| (vi) Combined valves                                   | 8    |
| (vii) Pentagrid converters                             | 8    |
| 4. MAXIMUM RATINGS AND TOLERANCES                      | 9    |
| (i) Maximum ratings and their interpretation           | 9    |
| (ii) Tolerances  | 9    |
| 5. FILAMENT AND HEATER VOLTAGE/CURRENT CHARACTERISTICS | 10   |
| 6. VALVE NUMBERING SYSTEMS                             | 10   |
| 7. REFERENCES  | 12   |
| <b>CHAPTER 2. VALVE CHARACTERISTICS</b>                |      |
| 1. VALVE COEFFICIENTS                                  | 13   |
| 2. CHARACTERISTIC CURVES                               | 15   |
| (i) Plate characteristics                              | 15   |
| (ii) Mutual characteristics                            | 17   |
| (iii) Grid current characteristics                     | 18   |
| (iv) Suppressor characteristics                        | 21   |
| (v) Constant current curves                            | 22   |
| (vi) "G" curves  | 23   |
| (vii) Drift of characteristics during life             | 23   |
| (viii) Effect of heater-voltage variation              | 24   |
| 3. RESISTANCE-LOADED AMPLIFIERS                        | 24   |
| (i) Triodes  | 24   |
| (ii) Pentodes  | 26   |
| 4. TRANSFORMER-COUPLED AMPLIFIERS                      | 27   |
| (i) With resistive load                                | 27   |
| (ii) Effect of primary resistance                      | 28   |
| (iii) With i-f voltage amplifiers                      | 28   |
| (iv) R-F amplifiers with sliding screen                | 28   |

## CONTENTS

| SECTION  | PAGE |
|--|------|
| (v) Cathode loadlines  | 29   |
| (vi) With reactive loads   | 30   |
| 5. TRIODE OPERATION OF PENTODES  | 34   |
| (i) Triode operation of pentodes   | 34   |
| (ii) Examples of transconductance calculation  | 34   |
| (iii) Triode amplification factor  | 35   |
| (iv) Plate resistance  | 36   |
| (v) Connection of suppressor grid  | 36   |
| 6. CONVERSION FACTORS, AND THE CALCULATION OF CHARACTERISTICS OTHER THAN THOSE PUBLISHED         | 36   |
| (i) The basis of valve conversion factors  | 36   |
| (ii) The use of valve conversion factors   | 37   |
| (iii) The calculation of valve characteristics other than those published                        | 40   |
| (iv) The effect of changes in operating conditions   | 42   |
| 7. VALVE EQUIVALENT CIRCUITS AND VECTORS   | 45   |
| (i) Constant voltage equivalent circuit  | 45   |
| (ii) Constant current equivalent circuit   | 46   |
| (iii) Valve vectors  | 47   |
| 8. VALVE ADMITTANCES   | 49   |
| (i) Grid input impedance and admittance  | 49   |
| (ii) Admittance coefficients   | 50   |
| (iii) The components of grid admittance-input resistance-input capacitance-grid input admittance | 51   |
| (iv) Typical values of short-circuit input conductance   | 55   |
| (v) Change of short-circuit-input capacitance with transconductance                              | 55   |
| (vi) Grid-cathode capacitance  | 56   |
| (vii) Input capacitances of pentodes (published values)  | 56   |
| (viii) Grid-plate capacitance  | 57   |
| 9. MATHEMATICAL RELATIONSHIPS  | 57   |
| (i) General  | 57   |
| (ii) Resistance load   | 58   |
| (iii) Power and efficiency   | 59   |
| (iv) Series expansion; resistance load   | 61   |
| (v) Series expansion; general case   | 63   |
| (vi) The equivalent plate circuit theorem  | 63   |
| (vii) Dynamic load line-general case-  | 64   |
| (viii) Valve networks-general case-  | 64   |
| (ix) Valve coefficients as partial differentials   | 64   |
| (x) Valve characteristics at low plate currents  | 65   |
| 10. REFERENCES   | 66   |

### CHAPTER 3. THE TESTING OF OXIDE-COATED CATHODE HIGH-VACUUM RECEIVING VALVES

|   |    |
|---|----|
| 1. BASIS OF TESTING PRACTICE                              | 68 |
| (i) Fundamental physical properties                       | 69 |
| (ii) Basic functional characteristics                     | 70 |
| (iii) Fundamental characteristic tests                    | 73 |
| (iv) Valve ratings and their limiting effect on operation | 75 |
| (A) Limiting ratings                                      | 75 |
| (B) Characteristics usually rated                         | 75 |
| (C) Rating systems  | 77 |
| (D) Interpretation of maximum ratings                     | 77 |
| (E) Operating conditions                                  | 80 |
| (v) Recommended practice and operation                    | 80 |
| (a) Mounting  | 80 |
| (b) Ventilation   | 81 |

## CONTENTS

| SECTION  | PAGE |
|--|------|
| (c) Heater-cathode insulation                                  | 81   |
| (d) Control grid circuit resistance                            | 82   |
| (e) Operation at low screen voltages                           | 84   |
| (f) Microphony   | 84   |
| (g) Hum  | 84   |
| (h) Stand-by operation   | 84   |
| <br>   |      |
| 2. CONTROL OF CHARACTERISTICS DURING MANUFACTURE               | 85   |
| (i) Importance of control over characteristics                 | 85   |
| (ii) Basic manufacturing test specification                    | 85   |
| (iii) Systematic testing                                       | 86   |
| (iv) Tolerances on characteristics                             | 88   |
| <br>   |      |
| 3. METHODS OF TESTING CHARACTERISTICS                          | 89   |
| (i) General conventions  | 90   |
| (ii) General characteristics                                   | 91   |
| (a) Physical dimensions  | 91   |
| (b) Shorts and continuity                                      | 91   |
| (c) Heater (or filament) current                               | 93   |
| (d) Heater to cathode leakage                                  | 94   |
| (e) Inter-electrode insulation                                 | 94   |
| (f) Emission   | 94   |
| (g) Direct inter-electrode capacitances                        | 95   |
| (iii) Specific diode characteristics                           | 99   |
| (a) Rectification test   | 99   |
| (b) Sputter and arcing   | 100  |
| (c) Back emission  | 100  |
| (d) Zero signal or standing diode current                      | 101  |
| (iv) Specific triode, pentode and beam tetrode characteristics | 101  |
| (A) Reverse grid current                                       | 101  |
| (B) Grid current commencement voltage                          | 102  |
| (C) Positive grid current                                      | 102  |
| (D) Positive voltage electrode currents                        | 103  |
| (E) Transconductance or mutual conductance                     | 103  |
| (F) Amplification factor                                       | 104  |
| (G) Plate resistance   | 104  |
| (H) A.C. amplification   | 105  |
| (I) Power output   | 105  |
| (J) Distortion   | 106  |
| (K) Microphony   | 107  |
| (L) Audio frequency noise                                      | 107  |
| (M) Radio frequency noise                                      | 107  |
| (N) Blocking   | 107  |
| (O) Stage gain testing   | 108  |
| (P) Electrode dissipation                                      | 108  |
| (v) Specific converter characteristics                         | 108  |
| (A) Methods of operation including oscillator excitation       | 108  |
| (1) Oscillator self-excited                                    | 108  |
| (2) Oscillator driven  | 109  |
| (3) Static operation   | 109  |
| (B) Specific characteristics                                   | 109  |
| (a) Reverse signal grid current                                | 109  |
| (b) Signal-grid current commencement                           | 109  |
| (c) Mixer positive voltage electrode currents                  | 109  |
| (d) Mixer conversion transconductance                          | 109  |
| (e) Mixer plate resistance                                     | 111  |
| (f) Mixer transconductance                                     | 111  |
| (g) Oscillator grid current                                    | 111  |

| <b>CONTENTS</b> |   | <b>PAGE</b> |
|-----------------|---|-------------|
| <b>SECTION</b>  |   |             |
|                 | (h) Oscillator plate current  | 113         |
|                 | (i) Oscillator transconductance   | 113         |
|                 | (j) Oscillator amplification factor   | 113         |
|                 | (k) Oscillator plate resistance   | 113         |
|                 | (l) Signal-grid blocking  | 113         |
|                 | (m) Microphony  | 113         |
|                 | (n) R-F noise   | 113         |
| (vi)            | Tests for special characteristics   | 113         |
|                 | (A) Short-circuit input admittance  | 113         |
|                 | (B) Short-circuit feedback admittance   | 117         |
|                 | (C) Short-circuit output admittance   | 117         |
|                 | (D) Short-circuit forward admittance  | 117         |
|                 | (E) Perveance   | 117         |
| (vii)           | Characteristics by pulse methods-point by point -                                   | 118         |
| (viii)          | Characteristics by curve tracer methods   | 119         |
| <b>4.</b>       | <b>ACCEPTANCE TESTING</b>   | <b>120</b>  |
|                 | (i) Relevant characteristics  | 120         |
|                 | (ii) Valve specifications   | 120         |
|                 | (iii) Testing procedure   | 120         |
| <b>5.</b>       | <b>SERVICE TESTING AND SERVICE TESTER PRACTICE</b>                                  | <b>121</b>  |
|                 | (i) Purpose and scope of service testing and discussion of as-<br>sociated problems | 121         |
|                 | (ii) Fundamental characteristics which should be tested                             | 122         |
|                 | (iii) Types of commercial testers   | 122         |
|                 | (iv) Methods of testing characteristics in commercial service testers               | 123         |
|                 | (a) Shorts testing  | 123         |
|                 | (b) Continuity testing  | 123         |
|                 | (c) Heater to cathode leakage   | 123         |
|                 | (d) Emission testing  | 123         |
|                 | (e) Mutual conductance testing  | 123         |
|                 | (f) Plate conductance testing   | 124         |
|                 | (g) Reverse grid current testing  | 124         |
|                 | (h) Power output testing  | 124         |
|                 | (i) Conversion conductance testing  | 124         |
|                 | (j) Oscillator mutual conductance testing   | 124         |
|                 | (k) Noise testing   | 124         |
|                 | (l) A.C. amplification testing  | 124         |
|                 | (v) A.C. versus d.c. electrode voltages in testers                                  | 124         |
|                 | (vi) Pre-heating  | 125         |
|                 | (vii) Testing procedure   | 125         |
| <b>6.</b>       | <b>REFERENCES</b>   | <b>125</b>  |

**PART 2: GENERAL THEORY AND COMPONENTS**  
**CHAPTER 4. THEORY OF NETWORKS**

|           |  |            |
|-----------|--|------------|
| <b>1.</b> | <b>CURRENT AND VOLTAGE</b>                     | <b>128</b> |
|           | (i) Direct current                             | 128        |
|           | (ii) Alternating current                       | 129        |
|           | (iii) Indications of polarity and current flow | 130        |
| <b>2.</b> | <b>RESISTANCE</b>                              | <b>130</b> |
|           | (i) Ohm's Law for d.c.                         | 130        |
|           | (ii) Ohm's Law for a.c.                        | 131        |
|           | (iii) Resistances in series                    | 131        |
|           | (iv) Resistances in parallel                   | 132        |
|           | (v) Conductance in resistive circuits          | 133        |

## CONTENTS

| SECTION  | PAGE |
|--|------|
| 3. POWER   | 133  |
| (i) Power in d.c. circuits   | 133  |
| (ii) Power in resistive a.c. circuits                                      | 133  |
| 4. CAPACITANCE   | 134  |
| (i) Introduction to capacitance  | 134  |
| (ii) Condensers in parallel and series                                     | 135  |
| (iii) Calculation of capacitance   | 135  |
| (iv) Condensers in d.c. circuits   | 136  |
| (v) Condensers in a.c. circuits  | 137  |
| 5. INDUCTANCE  | 140  |
| (i) Introduction to inductance   | 140  |
| (ii) Inductances in d.c. circuits  | 141  |
| (iii) Inductances in series and parallel                                   | 141  |
| (iv) Mutual inductance   | 142  |
| (v) Inductances in a.c. circuits   | 142  |
| (vi) Power in inductive circuits   | 143  |
| 6. IMPEDANCE AND ADMITTANCE  | 144  |
| (i) Impedance, a complex quantity  | 144  |
| (ii) Series circuits with L, C and R                                       | 144  |
| (iii) Parallel combinations of L, C and R                                  | 147  |
| (iv) Series-parallel combinations of L, C and R                            | 149  |
| (v) Conductance, susceptance and admittance                                | 153  |
| (vi) Conversion from series to parallel impedance                          | 157  |
| 7. NETWORKS  | 158  |
| (i) Introduction to networks   | 158  |
| (ii) Kirchhoff's Laws  | 160  |
| (iii) Potential dividers   | 161  |
| (iv) Thevenin's Theorem  | 164  |
| (v) Norton's Theorem   | 165  |
| (vi) Maximum Power Transfer Theorem  | 165  |
| (vii) Reciprocity Theorem  | 165  |
| (viii) Superposition Theorem   | 165  |
| (ix) Compensation Theorem  | 166  |
| (x) Four-terminal networks   | 166  |
| (xi) Multi-mesh networks   | 167  |
| (xii) Non-linear components in networks                                    | 170  |
| (xiii) Phase shift networks  | 170  |
| (xiv) Transients in networks   | 171  |
| (xv) References to networks  | 171  |
| 8. FILTERS   | 172  |
| (i) Introduction to filters  | 172  |
| (ii) Resistance-capacitance filters, high-pass and low-pass                | 172  |
| (iii) Special types of resistance-capacitance filters                      | 176  |
| (iv) Iterative impedances of four terminal networks                        | 176  |
| (v) Image impedances and image transfer constant of four terminal networks | 177  |
| (vi) Symmetrical networks  | 179  |
| (vii) "Constant k " filters  | 179  |
| (viii) M-derived filters   | 182  |
| (ix) Practical filters   | 184  |
| (x) Frequency dividing networks  | 184  |
| (xi) References to filters   | 185  |

## CONTENTS

| SECTION   | PAGE |
|---|------|
| 9. PRACTICAL RESISTORS, CONDENSERS AND INDUCTORS        | 186  |
| (i) Practical resistors                                 | 186  |
| (ii) Practical condensers                               | 191  |
| (iii) Combination units                                 | 197  |
| (iv) Practical inductors                                | 197  |
| (v) References to practical resistors and condensers    | 198  |
| <b>CHAPTER 5. TRANSFORMERS AND IRON-CORED INDUCTORS</b> |      |
| 1. IDEAL TRANSFORMERS                                   | 199  |
| (i) Definitions   | 199  |
| (ii) Impedance calculations-single load-                | 200  |
| (iii) Impedance calculations-multiple loads-            | 201  |
| 2. PRACTICAL TRANSFORMERS                               | 204  |
| (i) General considerations                              | 204  |
| (ii) Effects of losses                                  | 205  |
| 3. AUDIO-FREQUENCY TRANSFORMERS                         | 206  |
| (i) General considerations                              | 206  |
| (ii) Core materials                                     | 207  |
| (iii) Frequency response and distortion                 |      |
| (a) Interstage transformers                             | 209  |
| (b) Low level transformers                              | 210  |
| (c) Output transformers                                 | 211  |
| (iv) Designing for low leakage inductance               | 217  |
| (v) Winding capacitance                                 | 219  |
| (vi) Tests on output transformers                       | 227  |
| (vii) Specifications for a-f transformers               | 228  |
| 4. MAGNETIC CIRCUIT THEORY                              | 229  |
| (i) Fundamental magnetic relationships                  | 229  |
| (ii) The magnetic circuit                               | 231  |
| (iii) Magnetic units and conversion factors             | 232  |
| 5. POWER TRANSFORMERS                                   | 233  |
| (i) General   | 233  |
| (ii) Core material and size                             | 234  |
| (iii) Primary and secondary turns                       | 235  |
| (iv) Currents in windings                               | 236  |
| (v) Temperature rise                                    | 236  |
| (vi) Typical design                                     | 237  |
| (vii) Specifications for power transformers             | 241  |
| 6. IRON-CORED INDUCTORS                                 | 242  |
| (i) General   | 242  |
| (ii) Calculations-general-                              | 242  |
| (iii) Effective permeability                            | 243  |
| (iv) Design with no d.c. flux                           | 243  |
| (v) Design of high Q inductors                          | 245  |
| (vi) Design with d.c. flux                              | 247  |
| (vii) Design by Hanna's method                          | 248  |
| (viii) Design of inductors for choke-input filters      | 249  |
| (ix) Measurements                                       | 250  |
| (x) Iron-cored inductors in resonant circuits           | 251  |
| 7. REFERENCES   | 252  |

## CONTENTS

| SECTION                                       | CHAPTER 6. MATHEMATICS | PAGE |
|---|------------------------|------|
| 1. ARITHMETIC AND THE SLIDE RULE              |                        | 255  |
| (i) Figures                                   |                        | 255  |
| (ii) Powers and roots                         |                        | 255  |
| (iii) Logarithms                              |                        | 255  |
| (iv) The slide rule                           |                        | 257  |
| (v) Short cuts in arithmetic                  |                        | 258  |
| 2. ALGEBRA                                    |                        | 259  |
| (i) Addition                                  |                        | 260  |
| (ii) Subtraction                              |                        | 260  |
| (iii) Multiplication                          |                        | 260  |
| (iv) Division                                 |                        | 260  |
| (v) Powers                                    |                        | 260  |
| (vi) Roots                                    |                        | 261  |
| (vii) Brackets and simple manipulations       |                        | 261  |
| (viii) Factoring                              |                        | 262  |
| (ix) Proportion                               |                        | 262  |
| (x) Variation                                 |                        | 262  |
| (xi) Inequalities                             |                        | 262  |
| (xii) Functions                               |                        | 263  |
| (xiii) Equations                              |                        | 263  |
| (xiv) Formulae and laws                       |                        | 265  |
| (xv) Continuity and limits                    |                        | 265  |
| (xvi) Progressions, sequences and series      |                        | 266  |
| (xvii) Logarithmic and exponential functions  |                        | 267  |
| (xviii) Infinite series                       |                        | 268  |
| (xix) Hyperbolic functions                    |                        | 269  |
| (xx) General approximations                   |                        | 271  |
| 3. GEOMETRY AND TRIGONOMETRY                  |                        | 272  |
| (i) Plane figures                             |                        | 272  |
| (ii) Surfaces and volumes of solids           |                        | 275  |
| (iii) Trigonometrical relationships           |                        | 275  |
| 4. PERIODIC PHENOMENA                         |                        | 278  |
| 5. GRAPHICAL REPRESENTATION AND $j$ NOTATION  |                        | 279  |
| (i) Graphs                                    |                        | 279  |
| (ii) Finding the equation to a curve          |                        | 281  |
| (iii) Three variables                         |                        | 281  |
| (iv) Vectors and $j$ notation                 |                        | 282  |
| 6. COMPLEX ALGEBRA AND DE MOIVRE'S THEOREM    |                        | 285  |
| (i) Complex algebra with regular coordinates  |                        | 285  |
| (ii) Complex algebra with polar coordinates   |                        | 286  |
| (iii) De Moivre's Theorem                     |                        | 287  |
| 7. DIFFERENTIAL AND INTEGRAL CALCULUS         |                        | 289  |
| (i) Slope and rate of change                  |                        | 289  |
| (ii) Differentiation                          |                        | 291  |
| (iii) Integration                             |                        | 294  |
| (iv) Taylor's Series                          |                        | 298  |
| (v) Maclaurin's Series                        |                        | 299  |
| 8. FOURIER SERIES AND HARMONICS               |                        | 299  |
| (i) Periodic waves and the Fourier Series     |                        | 299  |
| (ii) Other applications of the Fourier Series |                        | 302  |
| (iii) Graphical Harmonic Analysis             |                        | 302  |
| 9. REFERENCES                                 |                        | 304  |



## CONTENTS

| SECTION |  | PAGE |
|---------|--|------|
|         | <b>CHAPTER 7. NEGATIVE FEEDBACK</b>                                      |      |
| 1.      | <b>FUNDAMENTAL TYPES OF FEEDBACK</b>                                     | 306  |
|         | (i) Feedback positive and negative                                       | 306  |
|         | (ii) Negative voltage feedback at the mid-frequency                      | 307  |
|         | (iii) Negative current feedback at the mid-frequency                     | 312  |
|         | (iv) Bridge negative feedback at the mid-frequency                       | 313  |
|         | (v) Combined positive and negative at the mid-frequency                  | 314  |
|         | (vi) Comparison between different fundamental types at the mid-frequency | 315  |
| 2.      | <b>PRACTICAL FEEDBACK CIRCUITS</b>                                       | 316  |
|         | (i) The cathode follower   | 316  |
|         | (ii) The cathode degenerative amplifier and phase splitter               | 327  |
|         | (iii) Voltage feedback from secondary of output transformer              | 330  |
|         | (iv) Voltage feedback from plate-transformer input-                      | 332  |
|         | (v) Voltage feedback from plate-r.c.c. input-                            | 332  |
|         | (vi) Voltage feedback over two stages                                    | 334  |
|         | (vii) Voltage feedback over three stages                                 | 344  |
|         | (viii) Cathode coupled phase inverters and amplifiers                    | 347  |
|         | (ix) Hum   | 348  |
|         | (x) Some special features of feedback amplifiers                         | 352  |
|         | (xi) Combined positive and negative feedback                             | 352  |
|         | (xii) Choke-coupled phase inverter                                       | 355  |
| 3.      | <b>STABILITY, PHASE SHIFT AND FREQUENCY RESPONSE</b>                     | 356  |
|         | (i) Stability and instability  | 356  |
|         | (ii) Conditions for stability  | 356  |
|         | (iii) Relationship between phase shift and attenuation                   | 359  |
|         | (iv) Design of 1 and 2 stage amplifiers                                  | 364  |
|         | (v) Design of multistage amplifiers                                      | 365  |
|         | (vi) Effect of feedback on frequency response                            | 378  |
|         | (vii) Design of amplifiers with flat frequency response                  | 379  |
|         | (viii) Constancy of characteristics with feedback                        | 388  |
|         | (ix) Effect of feedback on phase shift                                   | 389  |
| 4.      | <b>SPECIAL APPLICATIONS OF FEEDBACK</b>                                  | 389  |
| 5.      | <b>VALVE CHARACTERISTICS AND FEEDBACK</b>                                | 390  |
|         | (i) Triode cathode follower  | 390  |
|         | (ii) Pentode cathode follower  | 393  |
|         | (iii) Triode with voltage feedback                                       | 394  |
|         | (iv) Pentode with voltage feedback, transformer coupled                  | 395  |
|         | (v) Cathode degenerative triode  | 397  |
|         | (vi) Cathode degenerative pentode  | 399  |
|         | (vii) Cathode-coupled triodes  | 399  |
|         | (viii) Feedback over two stages  | 399  |
| 6.      | <b>REFERENCES TO FEEDBACK</b>  | 399  |
| 7.      | <b>OVERLOADING OF FEEDBACK AMPLIFIERS ON TRANSIENTS</b>                  | 1477 |
|         | <b>CHAPTER 8. WAVE MOTION AND THE THEORY OF MODULATION</b>               |      |
| 1.      | <b>INTRODUCTION TO ELECTROMAGNETIC WAVES</b>                             | 403  |
|         | (i) Wave motion  | 403  |
|         | (ii) Electromagnetic spectrum  | 404  |
|         | (iii) Wave propagation   | 404  |
| 2.      | <b>TRANSMISSION OF INTELLIGENCE</b>                                      | 405  |
|         | (i) Introduction   | 405  |
|         | (ii) Radio telegraphy  | 405  |
|         | (iii) Radio telephony  | 405  |
| 3.      | <b>REFERENCES</b>  | 406  |

## CONTENTS

| SECTION |   | PAGE |
|---------|---|------|
|         | <b>CHAPTER 9. TUNED CIRCUITS</b>                                    |      |
| 1.      | INTRODUCTION  | 407  |
| 2.      | DAMPED OSCILLATIONS   | 408  |
| 3.      | SERIES RESONANCE  | 409  |
| 4.      | PARALLEL RESONANCE  | 410  |
| 5.      | GENERAL CASE OF SERIES RESONANCE                                    | 412  |
| 6.      | SELECTIVITY AND GAIN  | 412  |
|         | (i) Single tuned circuit  | 412  |
|         | (ii) Coupled circuits-tuned secondary-                              | 413  |
|         | (iii) Coupled circuits-tuned primary, tuned secondary-              | 414  |
|         | (iv) Coupled circuits of equal Q                                    | 415  |
|         | (v) Coupled circuits of unequal Q                                   | 416  |
| 7.      | SELECTIVITY-GRAPHICAL METHODS-                                      | 416  |
|         | (i) Single tuned circuit  | 416  |
|         | (ii) Two identical coupled tuned circuits                           | 417  |
| 8.      | COUPLING OF CIRCUITS  | 418  |
|         | (i) Mutual inductive coupling                                       | 418  |
|         | (ii) Miscellaneous methods of coupling                              | 418  |
|         | (iii) Complex coupling  | 420  |
| 9.      | RESPONSE OF IDENTICAL AMPLIFIER STAGES IN CASCADE                   | 421  |
| 10.     | UNIVERSAL SELECTIVITY CURVES  | 421  |
| 11.     | SUMMARY OF FORMULAE FOR TUNED CIRCUITS                              | 423  |
| 12.     | REFERENCES  | 427  |
|         | <b>CHAPTER 10. CALCULATION OF INDUCTANCE</b>                        |      |
| 1.      | SINGLE LAYER COILS OR SOLENOIDS                                     | 429  |
|         | (i) Current-sheet inductance  | 429  |
|         | (ii) Solenoids wound with spaced round wires                        | 430  |
|         | (iii) Approximate formulae  | 432  |
|         | (iv) Design of single layer solenoid                                | 433  |
|         | (v) Magnitude of the differences between $L_s$ and $L_o$            | 435  |
|         | (vi) Curves for the determination of the "current-sheet" inductance | 437  |
|         | (vii) Effect of concentric, non-magnetic screen                     | 438  |
| 2.      | MULTILAYER SOLENOIDS  | 441  |
|         | (i) Formula for current sheet inductance                            | 441  |
|         | (ii) Correction for insulation thickness                            | 442  |
|         | (iii) Approximate formulae  | 442  |
|         | (iv) Design of multilayer coils                                     | 443  |
|         | (v) Effect of a concentric screen                                   | 444  |
| 3.      | TOROIDAL COILS  | 445  |
|         | (i) Toroidal coil of circular section with single layer winding     | 445  |
|         | (ii) Toroidal coil of rectangular section with single layer winding | 445  |
|         | (iii) Toroidal coil of rectangular section with multilayer winding  | 445  |
| 4.      | FLAT SPIRALS  | 445  |
|         | (i) Accurate formulae   | 445  |
|         | (ii) Approximate formulae   | 446  |
| 5.      | MUTUAL INDUCTANCE   | 446  |
|         | (i) Accurate methods  | 446  |
|         | (ii) Approximate methods  | 448  |
| 6.      | LIST OF SYMBOLS   | 448  |
| 7.      | REFERENCES  | 448  |

## CONTENTS

| SECTION |   | PAGE |
|---------|---|------|
|         | <b>CHAPTER 11. DESIGN OF RADIO FREQUENCY INDUCTORS</b>                    |      |
| 1.      | INTRODUCTION  | 450  |
| 2.      | SELF-CAPACITANCE OF COILS   | 451  |
|         | (i) Effects of self-capacitance   | 451  |
|         | (ii) Calculation of self-capacitance of single-layer solenoids            | 451  |
|         | (iii) Measurement of self-capacitance                                     | 453  |
| 3.      | INTERMEDIATE-FREQUENCY WINDINGS   | 453  |
|         | (i) Air-cored coils   | 453  |
|         | (ii) Iron-cored coils   | 454  |
|         | (iii) Expanding selectivity i-f transformers                              | 455  |
|         | (iv) Calculation of gear ratios for universal coils                       | 456  |
|         | (v) Miscellaneous considerations  | 458  |
| 4.      | MEDIUM WAVE-BAND COILS  | 459  |
|         | (i) Air-cored coils   | 459  |
|         | (ii) Iron-cored coils   | 460  |
|         | (iii) Permeability tuning   | 461  |
|         | (iv) Matching   | 462  |
| 5.      | SHORT-WAVE COILS  | 463  |
|         | (i) Design  | 463  |
|         | (ii) Miscellaneous features   | 468  |
| 6.      | RADIO-FREQUENCY CHOKES  | 474  |
|         | (i) Pie-wound chokes  | 474  |
|         | (ii) Other types  | 475  |
| 7.      | TROPIC PROOFING   | 476  |
|         | (i) General considerations  | 476  |
|         | (ii) Baking   | 476  |
|         | (iii) Impregnation  | 477  |
|         | (iv) Flash dipping  | 477  |
|         | (v) Materials   | 477  |
| 8.      | REFERENCES  | 478  |
|         | <b>PART 3: AUDIO FREQUENCIES</b>  |      |
|         | <b>CHAPTER 12. AUDIO FREQUENCY VOLTAGE AMPLIFIERS</b>                     |      |
| 1.      | INTRODUCTION  | 481  |
|         | (i) Voltage amplifiers  | 481  |
| 2.      | RESISTANCE-CAPACITANCE COUPLED TRIODES                                    | 482  |
|         | (i) Choice of operating conditions  | 482  |
|         | (ii) Coupling condenser   | 483  |
|         | (iii) Cathode bias  | 484  |
|         | (iv) Fixed bias   | 487  |
|         | (v) Grid leak bias  | 489  |
|         | (vi) Plate voltage and current  | 489  |
|         | (vii) Gain and distortion at the mid-frequency                            | 490  |
|         | (viii) Dynamic characteristics  | 491  |
|         | (ix) Maximum voltage output and distortion                                | 491  |
|         | (x) Conversion factors with r.c.c. triodes                                | 493  |
|         | (xi) Input impedance and Miller effect                                    | 493  |
|         | (xii) Equivalent circuit of r.c.c. triode                                 | 494  |
|         | (xiii) Voltage gain and phase shift                                       | 494  |
|         | (xiv) Comments on tabulated characteristics of resistance-coupled triodes | 495  |

## CONTENTS

| SECTION  | PAGE |
|--|------|
| 3. RESISTANCE-CAPACITANCE COUPLED PENTODES                                   | 496  |
| (i) Choice of operating conditions   | 496  |
| (ii) Coupling condenser  | 496  |
| (iii) Screen by-pass   | 496  |
| (iv) Cathode bias  | 499  |
| (v) Fixed bias   | 501  |
| (vi) Dynamic characteristics of pentodes                                     | 504  |
| (vii) Gain at the mid-frequency  | 506  |
| (viii) Dynamic characteristics of pentodes and comparison with triodes       | 508  |
| (ix) Maximum voltage output and distortion                                   | 510  |
| (x) Conversion factors with r.c.c. pentodes                                  | 511  |
| (xi) Equivalent circuit of r.c.c. pentode                                    | 512  |
| (xii) Voltage gain and phase shift   | 512  |
| (xiii) Screen loadlines  | 513  |
| (xiv) Combined screen and cathode loadlines and the effect of tolerances     | 515  |
| (xv) Remote cut-off pentodes as r.c.c. amplifiers                            | 516  |
| (xvi) Multigrid valves as r.c.c. amplifiers                                  | 516  |
| (xvii) Special applications  | 516  |
| (xviii) Comments on tabulated characteristics of resistance-coupled pentodes | 517  |
| 4. TRANSFORMER-COUPLED VOLTAGE AMPLIFIERS                                    | 517  |
| (i) Introduction   | 517  |
| (ii) Gain at the mid-frequency   | 517  |
| (iii) Gain at low frequencies  | 517  |
| (iv) Desirable valve characteristics   | 517  |
| (v) Equivalent circuits  | 518  |
| (vi) Gain and phase shift at all frequencies                                 | 518  |
| (vii) Transformer characteristics  | 518  |
| (viii) Fidelity  | 518  |
| (ix) Valve loadlines   | 518  |
| (x) Maximum peak output voltage  | 518  |
| (xi) Transformer loading   | 518  |
| (xii) Parallel feed  | 518  |
| (xiii) Auto-transformer coupling   | 520  |
| (xiv) Applications   | 520  |
| (xv) Special applications  | 520  |
| 5. CHOKE-COUPLED AMPLIFIERS  | 521  |
| (i) Performance  | 521  |
| (ii) Application   | 521  |
| 6. METHODS OF EXCITING PUSH-PULL AMPLIFIERS                                  | 521  |
| (i) Methods involving iron-cored inductors                                   | 521  |
| (ii) Phase splitter  | 522  |
| (iii) Phase inverter   | 524  |
| (iv) Self-balancing phase inverter   | 524  |
| (v) Self-balancing paraphase inverter  | 524  |
| (vi) Common cathode impedance self-balancing inverters                       | 526  |
| (vii) Balanced output amplifiers with highly accurate balance                | 527  |
| (viii) Cross coupled phase inverter  | 527  |
| 7. PUSH-PULL VOLTAGE AMPLIFIERS  | 527  |
| (i) Introduction   | 527  |
| (ii) Cathode resistors   | 527  |
| (iii) Output circuit   | 527  |
| (iv) Push-pull impedance-coupled amplifiers—mathematical treatment           | 528  |
| (v) Phase compressor   | 528  |

## CONTENTS

| SECTION  | PAGE |
|--|------|
| 8. IN-PHASE AMPLIFIERS   | 529  |
| (i) Cathode-coupled amplifiers                                   | 529  |
| (ii) Grounded-grid amplifiers                                    | 529  |
| (iii) Inverted input amplifiers                                  | 529  |
| (iv) Other forms of in-phase amplifiers                          | 529  |
| 9. DIRECT-COUPLED AMPLIFIERS                                     | 529  |
| (i) Elementary d-c amplifiers                                    | 529  |
| (ii) Bridge circuit  | 530  |
| (iii) Cathode-coupled  | 531  |
| (iv) Cathode follower  | 531  |
| (v) Phase inverter   | 532  |
| (vi) Screen coupled  | 532  |
| (vii) Gas tube coupled   | 532  |
| (viii) Modulation systems  | 532  |
| (ix) Compensated d.c. amplifiers                                 | 533  |
| (x) Bridge-balanced direct current amplifiers                    | 533  |
| (xi) Cascode amplifiers  | 533  |
| 10. STABILITY, DECOUPLING AND HUM                                | 535  |
| (i) Effect of common impedance in power supply                   | 535  |
| (ii) Plate supply by-passing                                     | 535  |
| (iii) Plate circuit decoupling                                   | 535  |
| (iv) Screen circuit decoupling                                   | 537  |
| (v) Grid circuit decoupling                                      | 538  |
| (vi) Hum in voltage amplifiers                                   | 538  |
| 11. TRANSIENTS AND PULSES IN AUDIO FREQUENCY AMPLIFIERS          | 540  |
| (i) Transient distortion   | 540  |
| (ii) Rectangular pulses  | 540  |
| 12. MULTISTAGE VOLTAGE AMPLIFIERS                                | 541  |
| (i) Single-channel amplifiers                                    | 541  |
| (ii) Multi-channel amplifiers                                    | 541  |
| 13. REFERENCES   | 542  |
| <b>CHAPTER 13. AUDIO FREQUENCY POWER AMPLIFIERS</b>              |      |
| 1. INTRODUCTION  | 544  |
| (i) Types of a-f power amplifiers                                | 544  |
| (ii) Class of operation  | 545  |
| (iii) Some characteristics of power amplifiers                   | 545  |
| (iv) Effect of power supply on power amplifiers                  | 547  |
| 2. CLASS A SINGLE TRIODES  | 548  |
| (i) Simplified graphical conditions, power output and distortion | 548  |
| (ii) General graphical case, power output and distortion         | 550  |
| (iii) Optimum operating conditions                               | 555  |
| (iv) Loudspeaker load  | 558  |
| (v) Plate circuit efficiency and power dissipation               | 559  |
| (vi) Power sensitivity   | 559  |
| (vii) Choke-coupled amplifier                                    | 559  |
| (viii) Effect of a.c. filament supply                            | 560  |
| (ix) Overloading   | 560  |
| (x) Regulation and by-passing of power supply                    | 560  |

## CONTENTS

| SECTION   | PAGE |
|---|------|
| 3. CLASS A MULTI-GRID VALVES  | 560  |
| (i) Introduction  | 560  |
| (ii) Ideal pentodes   | 561  |
| (iii) Practical pentodes—operating conditions-                              | 561  |
| (iv) Graphical analysis—power output and distortion-                        | 563  |
| (v) Rectification effects   | 565  |
| (vi) Cathode bias   | 565  |
| (vii) Resistance and inductance of transformer primary                      | 566  |
| (viii) Loudspeaker load   | 566  |
| (ix) Effects of plate and screen regulation                                 | 568  |
| (x) Beam power valves   | 569  |
| (xi) Space charge tetrodes  | 569  |
| (xii) Partial triode (" ultra-linear ") operation of pentodes               | 570  |
| 4. PARALLEL CLASS A AMPLIFIERS  | 570  |
| 5. PUSH-PULL TRIODES CLASS A, AB <sub>1</sub>                               | 571  |
| (i) Introduction  | 571  |
| (ii) Theory of push-pull amplification                                      | 573  |
| (iii) Power output and distortion   | 577  |
| (iv) Average plate current  | 579  |
| (v) Matching and the effects of mismatching                                 | 580  |
| (vi) Cathode bias   | 582  |
| (vii) Parasitics  | 582  |
| 6 PUSH-PULL PENTODES AND BEAM POWER AMPLIFIERS, CLASS A, AB <sub>1</sub>    | 583  |
| (i) Introduction  | 583  |
| (ii) Power output and distortion  | 583  |
| (iii) The effect of power supply regulation                                 | 584  |
| (iv) Matching and the effects of mismatching                                | 584  |
| (v) Average plate and screen currents                                       | 584  |
| (vi) Cathode bias   | 585  |
| (vii) Parasitics  | 585  |
| (viii) Phase inversion in the power stage                                   | 585  |
| (ix) Extended Class A   | 587  |
| (x) Partial triode (" ultra-linear ") operation                             | 587  |
| 7. CLASS B AMPLIFIERS AND DRIVERS   | 587  |
| (i) Introduction  | 587  |
| (ii) Power output and distortion—ideal conditions—Class B <sub>2</sub>      | 588  |
| (iii) Power output and distortion—practical conditions—Class B <sub>2</sub> | 588  |
| (iv) Grid driving conditions  | 590  |
| (v) Design procedure for Class B <sub>2</sub> amplifiers                    | 592  |
| (vi) Earthed-grid cathode coupled amplifiers                                | 592  |
| (vii) Class B <sub>1</sub> amplifiers—quiescent push-pull                   | 592  |
| 8. CLASS AB <sub>2</sub> AMPLIFIERS   | 593  |
| (i) Introduction  | 593  |
| (ii) Bias and screen stabilized Class AB <sub>2</sub> amplifier             | 593  |
| (iii) McIntosh amplifier  | 594  |
| 9. CATHODE-FOLLOWER POWER AMPLIFIERS  | 596  |
| 10. SPECIAL FEATURES  | 596  |
| (i) Grid circuit resistance   | 596  |
| (ii) Grid bias sources  | 597  |
| (iii) Miller Effect   | 598  |
| (iv) 26 volt operation  | 598  |
| (v) Hum from plate and screen supplies                                      | 599  |
| 11. COMPLETE AMPLIFIERS   | 599  |
| (i) Introduction  | 599  |
| (ii) Design procedure and examples  | 599  |
| (iii) Loudspeaker load  | 600  |
| 12. REFERENCES  | 601  |

## CONTENTS

| SECTION  | CHAPTER 14. FIDELITY AND DISTORTION | PAGE |
|--|-------------------------------------|------|
| 1. INTRODUCTION  |                                     | 603  |
| (i) Fidelity   |                                     | 603  |
| (ii) Types of distortion                               |                                     | 604  |
| (iii) Imagery for describing reproduced sound          |                                     | 604  |
| 2. NON-LINEAR DISTORTION AND HARMONICS                 |                                     | 605  |
| (i) Non-linearity                                      |                                     | 605  |
| (ii) Harmonics   |                                     | 606  |
| (iii) Permissible harmonic distortion                  |                                     | 607  |
| (iv) Total harmonic distortion                         |                                     | 609  |
| (v) Weighted distortion factor                         |                                     | 610  |
| (vi) The search for a true criterion of non-linearity  |                                     | 610  |
| 3. INTERMODULATION DISTORTION                          |                                     | 611  |
| (i) Introduction                                       |                                     | 611  |
| (ii) Modulation method of measurement—r.m.s. sum       |                                     | 612  |
| (iii) Difference frequency intermodulation method      |                                     | 613  |
| (iv) Individual side-band method                       |                                     | 613  |
| (v) Modulation method of measurement—peak sum          |                                     | 614  |
| (vi) Le Bel's oscillographic method                    |                                     | 614  |
| (vii) Comparison between different methods             |                                     | 616  |
| (viii) Synthetic bass                                  |                                     | 616  |
| 4. FREQUENCY DISTORTION                                |                                     | 617  |
| (i) Frequency range                                    |                                     | 617  |
| (ii) Tonal balance                                     |                                     | 617  |
| (iii) Minimum audible change in frequency range        |                                     | 617  |
| (iv) Sharp peaks                                       |                                     | 618  |
| 5. PHASE DISTORTION                                    |                                     | 618  |
| 6. TRANSIENT DISTORTION                                |                                     | 619  |
| (i) General survey                                     |                                     | 619  |
| (ii) Testing for transient response                    |                                     | 619  |
| 7. DYNAMIC RANGE AND ITS LIMITATIONS                   |                                     | 620  |
| (i) Volume range and hearing                           |                                     | 620  |
| (ii) Effect of volume level on frequency range         |                                     | 621  |
| (iii) Acoustical power and preferred listening levels  |                                     | 623  |
| (iv) Volume range in musical reproduction              |                                     | 623  |
| (v) The effect of noise                                |                                     | 624  |
| 8. SCALE DISTORTION                                    |                                     | 625  |
| 9. OTHER FORMS OF DISTORTION                           |                                     | 626  |
| (i) Frequency-modulation distortion                    |                                     | 626  |
| (ii) Variation of frequency response with output level |                                     | 626  |
| (iii) Listener fatigue                                 |                                     | 626  |
| 10. FREQUENCY RANGE PREFERENCES                        |                                     | 627  |
| (i) Tests by Chinn and Eisenberg                       |                                     | 627  |
| (ii) Tests by Olson                                    |                                     | 627  |
| (iii) Single channel versus dual-channel tests         |                                     | 627  |
| (iv) Summing up  |                                     | 628  |
| 11. SPEECH REPRODUCTION                                |                                     | 628  |
| (i) The characteristics of speech                      |                                     | 628  |
| (ii) Articulation                                      |                                     | 628  |
| (iii) Masking of speech by noise                       |                                     | 629  |
| (iv) Distortion in speech reproduction                 |                                     | 629  |
| (v) Frequency ranges for speech                        |                                     | 630  |

## CONTENTS

| SECTION                              | PAGE |
|--------------------------------------|------|
| 12. HIGH FIDELITY REPRODUCTION       | 630  |
| (i) The target of high fidelity      | 630  |
| (ii) Practicable high fidelity       | 630  |
| (iii) The ear as a judge of fidelity | 632  |
| 13. REFERENCES                       | 632  |

### CHAPTER 15. TONE COMPENSATION AND TONE CONTROL

|  |     |
|--|-----|
| 1. INTRODUCTION  | 635 |
| (i) The purpose of tone compensation                       | 635 |
| (ii) Tone control  | 636 |
| (iii) General considerations                               | 636 |
| (iv) Distortion due to tone control                        | 636 |
| (v) Calculations involving decibels per octave             | 637 |
| (vi) Attenuation expressed as a time constant              | 638 |
| (vii) The elements of tone control filters                 | 639 |
| (viii) Fundamental circuit incorporating R and C           | 639 |
| (ix) Damping of tuned circuits                             | 639 |
| (x) Tolerances of elements                                 | 639 |
| 2. BASS BOOSTING   | 640 |
| (i) General remarks  | 640 |
| (ii) Circuits not involving resonance or negative feedback | 640 |
| (iii) Methods incorporating resonant circuits              | 644 |
| (iv) Circuits involving feedback                           | 645 |
| (v) Regeneration due to negative resistance characteristic | 648 |
| 3. BASS ATTENUATION  | 649 |
| (i) General remarks  | 649 |
| (ii) Bass attenuation by grid coupling condensers          | 649 |
| (iii) Bass attenuation by cathode resistor by-passing      | 649 |
| (iv) Bass attenuation by screen by-passing                 | 650 |
| (v) Bass attenuation by reactance shunting                 | 650 |
| (vi) Bass attenuation by negative feedback                 | 651 |
| (vii) Bass attenuation by Parallel-T network               | 651 |
| (viii) Bass attenuation using Constant k filters           | 652 |
| (ix) Bass attenuation using M-derived filters              | 652 |
| 4. COMBINED BASS TONE CONTROLS                             | 653 |
| (i) Stepped controls                                       | 653 |
| (ii) Continuously variable controls                        | 653 |
| 5. TREBLE BOOSTING   | 653 |
| (i) General remarks  | 653 |
| (ii) Circuits not involving resonance or negative feedback | 653 |
| (iii) Methods incorporating resonant circuits              | 654 |
| (iv) Circuits involving feedback                           | 655 |
| 6. TREBLE ATTENUATION                                      | 655 |
| (i) General remarks  | 655 |
| (ii) Attenuation by shunt capacitance                      | 655 |
| (iii) Treble attenuation by filter networks                | 657 |
| (iv) Treble attenuation in negative feedback amplifiers    | 657 |
| 7. COMBINED TREBLE TONE CONTROLS                           | 658 |
| 8. COMBINED BASS AND TREBLE TONE CONTROLS                  | 658 |
| (i) Stepped controls-general—                              | 658 |
| (ii) Quality switch  | 659 |
| (iii) Universal step-type tone control not using inductors | 660 |
| (iv) Universal step-type tone control using inductors      | 661 |
| (v) Fixed bass and treble boosting                         | 662 |



| <b>CONTENTS</b> |  | <b>PAGE</b> |
|-----------------|--|-------------|
| <b>SECTION</b>  |  |             |
|                 | (vi) Step-type tone control using negative feedback                                | 662         |
|                 | (vii) Continuously-variable controls—general                                       | 662         |
|                 | (viii) Single control continuously-variable tone controls                          | 662         |
|                 | (ix) Ganged continuously-variable tone controls                                    | 664         |
|                 | (x) Dual control continuously-variable tone controls                               | 664         |
| 9.              | <b>FEEDBACK TO PROVIDE TONE CONTROL</b>  | 669         |
|                 | (i) Introduction   | 669         |
|                 | (ii) Amplifiers with feedback providing tone control                               | 669         |
|                 | (iii) Whistle filters using feedback   | 672         |
| 10.             | <b>AUTOMATIC FREQUENCY-COMPENSATED VOLUME CONTROL</b>                              | 672         |
|                 | (i) Introduction   | 672         |
|                 | (ii) Methods incorporating a tapped potentiometer                                  | 672         |
|                 | (iii) Methods incorporating step-type controls                                     | 673         |
|                 | (iv) Method incorporating inverse volume expansion with<br>multi-channel amplifier | 673         |
| 11.             | <b>WHISTLE FILTERS</b>   | 673         |
|                 | (i) Resonant circuit filters   | 673         |
|                 | (ii) Narrow band rejection filter  | 675         |
|                 | (iii) Crystal filters  | 675         |
|                 | (iv) Parallel-T network  | 675         |
|                 | (v) Filters incorporating L and C  | 676         |
| 12.             | <b>OTHER METHODS OF TONE CONTROL</b>   | 676         |
|                 | (i) Multiple-channel amplifiers  | 676         |
|                 | (ii) Synthetic bass  | 676         |
| 13.             | <b>THE LISTENER AND TONE CONTROL</b>   | 677         |
| 14.             | <b>EQUALIZER NETWORKS</b>  | 677         |
| 15.             | <b>REFERENCES</b>  | 677         |

## **CHAPTER 16. VOLUME EXPANSION, COMPRESSION AND LIMITING**

|    |  |     |
|----|--|-----|
| 1. | <b>GENERAL PRINCIPLES</b>                                  | 679 |
|    | (i) Introduction   | 679 |
|    | (ii) An ideal system                                       | 680 |
|    | (iii) Practical problems in volume expansion               | 680 |
|    | (iv) Distortion  | 681 |
|    | (v) General comments                                       | 681 |
| 2. | <b>VOLUME COMPRESSION</b>                                  | 681 |
|    | (i) Introduction   | 681 |
|    | (ii) Peak limiters   | 682 |
|    | (iii) Volume limiters                                      | 683 |
|    | (iv) Distortion caused by peak limiters or volume limiters | 683 |
|    | (v) Volume compression                                     | 683 |
|    | (vi) Volume compression plus limiting                      | 684 |
|    | (vii) Compression of commercial speech                     | 684 |
| 3. | <b>GAIN CONTROL DEVICES</b>                                | 684 |
|    | (i) Remote cut-off pentodes                                | 684 |
|    | (ii) Pentagrids and triode-hexodes                         | 685 |
|    | (iii) Plate resistance control                             | 685 |
|    | (iv) Negative feedback                                     | 685 |
|    | (v) Lamps  | 685 |
|    | (vi) Suppressor-grid control                               | 686 |

## CONTENTS

| SECTION  | PAGE |
|--|------|
| 4. VOLUME EXPANSION  | 686  |
| (i) Introduction   | 686  |
| (ii) Expanders incorporating lamps                               | 687  |
| (iii) Expanders utilizing feedback                               | 688  |
| (iv) Expanders incorporating remote cut-off pentodes             | 688  |
| (v) Expanders incorporating remote cut-off triodes               | 689  |
| (vi) Expanders incorporating suppressor-grid controlled pentodes | 689  |
| (vii) Expanders incorporating valves with five grids             | 691  |
| (viii) Expanders incorporating plate resistance control          | 692  |
| 5. PUBLIC ADDRESS A.V.C.   | 693  |
| 6. SPEECH CLIPPERS   | 693  |
| 7. NOISE PEAK AND OUTPUT LIMITERS                                | 694  |
| (i) Introduction   | 694  |
| (ii) Instantaneous noise peak limiters                           | 694  |
| (iii) Output limiters  | 698  |
| (iv) General remarks   | 699  |
| 8. REFERENCES  | 699  |
| <br><b>CHAPTER 17. REPRODUCTION FROM RECORDS</b>                 |      |
| 1. INTRODUCTION TO DISC RECORDING                                | 701  |
| (i) Methods used in sound recording                              | 701  |
| (ii) Principles of lateral recording                             | 702  |
| (iii) Frequency range  | 704  |
| (iv) Surface noise and dynamic range                             | 704  |
| (v) Processing   | 705  |
| (vi) Turntables and driving mechanism                            | 705  |
| (vii) Automatic record changers                                  | 705  |
| 2. DISCS AND STYLI   | 706  |
| (i) General information on discs                                 | 706  |
| (ii) Dimensions of records and grooves                           | 706  |
| (iii) Styli  | 709  |
| (iv) Pinch effect  | 711  |
| (v) Radius compensation  | 711  |
| (vi) Record and stylus wear                                      | 712  |
| 3. PICKUPS   | 714  |
| (i) General survey   | 714  |
| (ii) Electro-magnetic (moving iron) pickups                      | 717  |
| (iii) Dynamic (moving coil) pickups                              | 719  |
| (iv) Piezo-electric (crystal) pickups                            | 720  |
| (v) Magnetostriction pickups                                     | 721  |
| (vi) Strain-sensitive pickups                                    | 721  |
| (vii) Ribbon pickups   | 722  |
| (viii) Capacitance pickups                                       | 722  |
| (ix) Eddy-current pickups  | 723  |
| 4. TRACKING  | 723  |
| (i) General survey of the problem                                | 723  |
| (ii) How to design for minimum distortion                        | 725  |
| (iii) The influence of stylus friction                           | 726  |
| 5. RECORDING CHARACTERISTICS, EQUALIZERS AND AMPLIFIERS          | 727  |
| (i) Recording characteristics                                    | 727  |
| (ii) Pre-amplifiers for use with pickups                         | 732  |
| (iii) Introduction to equalizers                                 | 732  |
| (iv) High-frequency attenuation (scratch filter)                 | 737  |
| (v) Equalizers for electro-magnetic pickups                      | 738  |

## CONTENTS

| SECTION  | PAGE |
|--|------|
| (vi) Equalizers for crystal pickups                          | 741  |
| (vii) Equalizers applying negative feedback to the pickup    | 743  |
| (viii) Miscellaneous details regarding equalizing amplifiers | 743  |
| (ix) Complete amplifiers                                     | 744  |
| (x) Pickups for connection to radio receivers                | 751  |
| (xi) Frequency test records                                  | 752  |
| 6. DISTORTION AND UNDESIRABLE EFFECTS                        | 757  |
| (i) Tracing distortion and pinch effect                      | 757  |
| (ii) Playback loss   | 760  |
| (iii) Wow, and the effects of record warping                 | 760  |
| (iv) Distortion due to stylus wear                           | 761  |
| (v) Noise modulation   | 761  |
| (vi) Pickup distortion                                       | 762  |
| (vii) Acoustical radiation                                   | 762  |
| (viii) Distortion in recording                               | 762  |
| 7. NOISE REDUCTION   | 763  |
| (i) Analysis of noise  | 763  |
| (ii) High-frequency attenuation                              | 763  |
| (iii) High-frequency pre-emphasis and de-emphasis            | 763  |
| (iv) Volume expansion  | 763  |
| (v) Olson noise suppressor                                   | 763  |
| (vi) Scott dynamic noise suppressor                          | 764  |
| (vii) Price balanced clipper noise suppressor                | 765  |
| 8. LACQUER DISC HOME RECORDING (DIRECT PLAYBACK)             | 766  |
| (i) General description                                      | 766  |
| (ii) Recording characteristic                                | 766  |
| (iii) Cutting stylus   | 767  |
| (iv) Cutter head   | 767  |
| (v) Equalization of cutter                                   | 767  |
| (vi) Motor and turntable                                     | 767  |
| (vii) Amplifier  | 767  |
| (viii) Pickups for use on lacquer discs                      | 768  |
| (ix) Recording with embossed groove                          | 768  |
| 9. REPRODUCTION FROM TRANSCRIPTION DISCS                     | 769  |
| (i) Introduction   | 769  |
| (ii) Characteristics of record material, wear and noise      | 769  |
| (iii) Sound track  | 770  |
| (iv) Recording characteristics and equalization              | 770  |
| (v) Translation loss and radius compensation                 | 770  |
| 10. REFERENCES TO LATERAL DISC RECORDING                     | 771  |

### CHAPTER 18. MICROPHONES, PRE-AMPLIFIERS, ATTENUATORS AND MIXERS

|                                       |     |
|---------------------------------------|-----|
| 1. MICROPHONES                        | 775 |
| (i) General survey                    | 775 |
| (ii) Carbon microphones               | 777 |
| (iii) Condenser microphones           | 778 |
| (iv) Crystal and ceramic microphones  | 778 |
| (v) Moving coil (dynamic) microphones | 779 |
| (vi) Pressure ribbon microphones      | 779 |
| (vii) Velocity ribbon microphones     | 779 |
| (viii) Throat microphones             | 780 |
| (ix) Lapel microphones                | 780 |
| (x) Lip microphones                   | 780 |

## CONTENTS

| SECTION   | PAGE |
|---|------|
| (xi) The directional characteristics of microphones                   | 780  |
| (xii) The equalization of microphones                                 | 781  |
| (xiii) Microphone transformers  | 781  |
| (xiv) Standards for microphones                                       | 781  |
| 2. PRE-AMPLIFIERS   | 782  |
| (i) Introduction  | 782  |
| (ii) Noise  | 782  |
| (iii) Hum   | 784  |
| (iv) Microphony   | 786  |
| (v) Valves for use in pre-amplifiers                                  | 786  |
| (vi) Microphone pre-amplifiers  | 788  |
| (vii) Pickup pre-amplifiers   | 793  |
| (viii) Gain-controlled pre-amplifiers                                 | 793  |
| (ix) Standard pre-amplifiers for broadcasting                         | 793  |
| (x) Standard pre-amplifiers for sound equipment                       | 793  |
| 3. ATTENUATORS AND MIXERS   | 794  |
| (i) Potentiometer type attenuators (volume controls)                  | 794  |
| (ii) Single section attenuators-constant impedance—                   | 795  |
| (iii) Single section attenuators-constant impedance in one direction— |      |
| only  | 795  |
| (iv) Multiple section attenuators                                     | 796  |
| (v) Electronic attenuators  | 797  |
| (vi) Mixers and faders—general  | 798  |
| (vii) Non-constant impedance mixers and faders                        | 798  |
| (viii) Constant impedance mixers and faders                           | 801  |
| 4. REFERENCES   | 804  |

## CHAPTER 19. UNITS FOR THE MEASUREMENT OF GAIN AND NOISE

|  |     |
|--|-----|
| 1. BELS AND DECIBELS   | 806 |
| (i) Power relationships expressed in bels and decibels             | 806 |
| (ii) Voltage and current relationships expressed in decibels       | 807 |
| (iii) Absolute power and voltage expressed in decibels             | 807 |
| (iv) Microphone output expressed in decibels                       | 808 |
| (v) Pickup output expressed in decibels                            | 810 |
| (vi) Amplifier gain expressed in decibels                          | 810 |
| (vii) Combined microphone and amplifier gain expressed in decibels | 811 |
| (viii) Loudspeaker output expressed in decibels                    | 812 |
| (ix) Sound system rating   | 812 |
| (x) Tables and charts of decibel relationships                     | 813 |
| (xi) Nomogram for adding decibel-expressed quantities              | 821 |
| (xii) Decibels, slide rules and mental arithmetic                  | 822 |
| 2. VOLUME INDICATORS AND VOLUME UNITS                              | 823 |
| (i) Volume indicators  | 823 |
| (ii) Volume units  | 824 |
| 3. INDICATING INSTRUMENTS  | 825 |
| (i) Decibel meters   | 825 |
| (ii) Power output meters   | 825 |
| (iii) Volume indicators  | 825 |
| (iv) Acoustical instruments  | 825 |
| 4. NEPERS AND TRANSMISSION UNITS                                   | 825 |
| (i) Nepers   | 825 |
| (ii) Transmission units  | 826 |

## CONTENTS

| SECTION                                      | PAGE |
|--|------|
| 5. LOUDNESS                                  | 826  |
| (i) Introduction to loudness                 | 826  |
| (ii) The phon                                | 826  |
| (iii) Loudness units                         | 827  |
| 6. THE MEASUREMENT OF SOUND LEVEL AND NOISE  | 827  |
| (i) Introduction                             | 827  |
| (ii) The sound level meter                   | 828  |
| (iii) The measurement of noise in amplifiers | 829  |
| (iv) The measurement of radio noise          | 829  |
| 7. REFERENCES                                | 830  |

## CHAPTER 20. LOUSPEAKERS

|   |     |
|---|-----|
| 1. INTRODUCTION   | 831 |
| (i) Types of loudspeakers   | 831 |
| (ii) Direct radiator loudspeakers   | 831 |
| (iii) Horn loudspeakers   | 832 |
| (iv) Headphones   | 832 |
| (v) Loudspeaker characteristics   | 833 |
| (vi) Amplitude of cone movement   | 834 |
| (vii) Good qualities of loudspeakers  | 834 |
| (viii) Loudspeaker grilles  | 835 |
| 2. CHARACTERISTICS OF MOVING-COIL CONE LOUSPEAKERS                                      | 835 |
| (i) Rigid (piston) cone in an infinite flat baffle                                      | 835 |
| (ii) Practical cones  | 835 |
| (iii) Special constructions for wide frequency range                                    | 836 |
| (iv) Impedance and phase angle  | 837 |
| (v) Frequency response  | 838 |
| (vi) Efficiency   | 839 |
| (vii) Directional characteristics   | 839 |
| (viii) Field magnet   | 840 |
| (ix) Hum bucking coil   | 840 |
| (x) Damping   | 840 |
| 3. BAFFLES AND ENCLOSURES FOR DIRECT-RADIATOR LOUSPEAKERS                               | 842 |
| (i) Flat baffles  | 842 |
| (ii) Open back cabinets   | 842 |
| (iii) Enclosed cabinet loudspeakers   | 843 |
| (iv) Acoustical phase inverter ("vented baffle")  | 845 |
| (v) Acoustical labyrinth loudspeakers   | 850 |
| (vi) The R-J loudspeaker  | 850 |
| (vii) Design of exterior of cabinet   | 850 |
| 4. HORN LOUSPEAKERS   | 851 |
| (I) Introduction  | 851 |
| (ii) Conical horns  | 851 |
| (iii) Exponential horns   | 851 |
| (iv) Hyperbolic exponential horns   | 853 |
| (v) Horn loudspeakers-general—  | 854 |
| (vi) Folded horn loudspeakers   | 856 |
| (vii) High-frequency horns  | 858 |
| (viii) Combination horn and phase inverter loudspeakers for personal<br>radio receivers | 859 |
| (ix) Material for making horns  | 859 |
| 5. DUAL AND TRIPLE SYSTEM LOUSPEAKERS   | 860 |
| (i) Introduction  | 860 |
| (ii) Choice of the cross-over frequency   | 860 |

## CONTENTS

| SECTION  | PAGE |
|--|------|
| (iii) The overlap region                               | 861  |
| (iv) Compromise arrangements                           | 861  |
| 6. LOUDSPEAKERS IN OPERATION                           | 861  |
| (i) Loudness   | 861  |
| (ii) Power required                                    | 861  |
| (iii) Acoustics of rooms                               | 864  |
| (iv) Loudspeaker placement                             | 865  |
| (v) Stereophonic reproduction                          | 865  |
| (vi) Sound reinforcing systems                         | 866  |
| (vii) Open air Public Address                          | 867  |
| (viii) Inter-communicating systems                     | 867  |
| (ix) Background music in factories                     | 867  |
| 7. DISTORTION IN LOUDSPEAKERS                          | 868  |
| (i) Non-linearity                                      | 868  |
| (ii) Frequency-modulation distortion in loudspeakers   | 869  |
| (iii) Transient distortion                             | 869  |
| (iv) Sub-harmonics and sub-frequencies                 | 871  |
| (v) Intermodulation distortion                         | 871  |
| 8. SUMMARY OF ACOUSTICAL DATA                          | 871  |
| (i) Definitions in acoustics                           | 871  |
| (ii) Electrical, mechanical and acoustical equivalents | 872  |
| (iii) Velocity and wavelength of sound                 | 872  |
| (iv) Musical scales                                    | 873  |
| 9. STANDARDS FOR LOUDSPEAKERS                          | 874  |
| (i) Voice coil impedance for radio receivers           | 874  |
| (ii) Loudspeaker standard ratings for sound equipment  | 874  |
| 10. REFERENCES TO LOUDSPEAKERS                         | 876  |

### CHAPTER 21. THE NETWORK BETWEEN THE POWER VALVE AND THE LOUDSPEAKER

|   |     |
|---|-----|
| 1. LOUDSPEAKER "MATCHING"   | 880 |
| (i) Loudspeaker characteristics and matching                                    | 880 |
| (ii) Optimum plate resistance   | 880 |
| (iii) Procedure for " matching " loudspeakers to various types of<br>amplifiers | 881 |
| 2. MULTIPLE AND EXTENSION LOUDSPEAKERS  | 882 |
| (i) Multiple loudspeakers—general   | 882 |
| (ii) Sound systems  | 883 |
| (iii) Extension loudspeakers  | 883 |
| (iv) Operation of loudspeakers at long distances from amplifier                 | 886 |
| 3. LOUDSPEAKER DIVIDER NETWORKS   | 887 |
| 4. REFERENCES   | 889 |

### PART 4: RADIO FREQUENCIES CHAPTER 22. AERIALS AND TRANSMISSION LINES

|  |     |
|--|-----|
| 1. INTRODUCTION  | 890 |
| 2. THE TRANSMISSION LINE                                   | 890 |
| (i) Introduction   | 890 |
| (ii) The correct termination for a transmission line       | 890 |
| (iii) Impedance-transforming action of a transmission line | 891 |

## CONTENTS

| SECTION  | PAGE |
|--|------|
| 3. AERIALS AND POWER TRANSFER  | 892  |
| (i) Introduction   | 892  |
| (ii) Power transfer  | 892  |
| 4. CHARACTERISTICS OF AERIALS  | 893  |
| (i) Effective area of a receiving aerial   | 893  |
| (ii) The power gain of an aerial   | 894  |
| (iii) The beam-width of an aerial  | 894  |
| 5. EFFECTS OF THE EARTH ON THE PERFORMANCE OF AN AERIAL                                | 894  |
| (i) Introduction   | 894  |
| (ii) A perfectly-conducting earth  | 894  |
| (iii) An imperfectly conducting earth  | 896  |
| (iv) The attenuation of radio waves in the presence of an imperfectly-reflecting earth | 896  |
| 6. THE EFFECT OF THE IONOSPHERE ON THE RECEPTION OF RADIO SIGNALS                      | 901  |
| 7. THE IMPEDANCE OF AN AERIAL  | 901  |
| (i) Introduction   | 901  |
| (ii) Resistive component of impedance  | 902  |
| (iii) Reactive component of impedance  | 903  |
| (iv) Characteristic impedance of aerial  | 903  |
| (v) Examples of calculations   | 903  |
| (vi) Dipoles   | 904  |
| (vii) Loop aerials   | 905  |
| 8. DUMMY AERIALS   | 906  |
| 9. TYPES OF AERIAL USED FOR BROADCAST RECEPTION  | 907  |
| (i) Introduction   | 907  |
| (ii) Medium-frequency receiving aerials  | 907  |
| (iii) Short-wave receiving aerials   | 908  |
| (iv) V-H-F aerials   | 909  |
| 10. REFERENCES   | 911  |

## CHAPTER 23. RADIO FREQUENCY AMPLIFIERS

|  |     |
|--|-----|
| 1. INTRODUCTION                          | 912 |
| (i) Aerial coupling                      | 912 |
| (ii) Tuning methods                      | 913 |
| (iii) R-F amplifiers                     | 913 |
| (iv) Design considerations               | 914 |
| 2. AERIAL STAGES                         | 915 |
| (i) Difficulties involved                | 915 |
| (ii) Generalized coupling networks       | 915 |
| (iii) Mutual inductance coupling         | 916 |
| (iv) Tapped inductance                   | 920 |
| (v) Capacitance coupling                 | 921 |
| (vi) General summary                     | 921 |
| 3. R-F AMPLIFIERS                        | 922 |
| (i) Reasons for using r-f stage          | 922 |
| (ii) Mutual-inductance-coupled stage     | 922 |
| (iii) Parallel tuned circuit             | 923 |
| (iv) Choke-capacitance coupling          | 924 |
| (v) Untuned and pre-tuned stages         | 924 |
| (vi) Grounded grid stages                | 925 |
| 4. IMAGE REJECTION                       | 925 |
| (i) Meaning of image rejection           | 925 |
| (ii) Image rejection due to aerial stage | 926 |
| (iii) Other considerations               | 926 |

## CONTENTS

| SECTION   | PAGE |
|---|------|
| 5. EFFECTS OF VALVE INPUT ADMITTANCE                        | 927  |
| (i) Important general considerations                        | 927  |
| (ii) Input loading of receiving valves at radio frequencies | 928  |
| (A) Input conductance                                       | 929  |
| (B) Cold input conductance                                  | 929  |
| (C) Hot input conductance                                   | 930  |
| (D) Change in input capacitance                             | 932  |
| (E) Reduction of detuning effect                            | 933  |
| 6. VALVE AND CIRCUIT NOISE                                  | 935  |
| (i) Thermal agitation noise                                 | 935  |
| (ii) Shot noise   | 936  |
| (iii) Induced grid noise                                    | 939  |
| (iv) Total noise calculations                               | 940  |
| (v) Sample circuit calculations                             | 941  |
| (vi) Conclusions  | 942  |
| 7. INSTABILITY IN R-F AMPLIFIERS                            | 942  |
| (i) Causes of instability                                   | 942  |
| (ii) Inter-electrode capacitance coupling                   | 943  |
| (iii) Summary   | 944  |
| 8. DISTORTION   | 944  |
| (i) Modulation envelope distortion                          | 945  |
| (ii) Cross modulation distortion                            | 945  |
| 9. BIBLIOGRAPHY   | 945  |

## CHAPTER 24. OSCILLATORS

|   |     |
|---|-----|
| 1. INTRODUCTION                               | 947 |
| 2. TYPES OF OSCILLATOR CIRCUITS               | 949 |
| (i) Tuned plate oscillator                    | 949 |
| (ii) Tuned grid oscillator                    | 950 |
| (iii) Hartley oscillator                      | 951 |
| (iv) Colpitts oscillator                      | 952 |
| (v) Electron-coupled oscillator               | 953 |
| (vi) Negative transconductance oscillators    | 953 |
| 3. CLASS A <sub>1</sub> , B AND C OSCILLATORS | 954 |
| 4. CAUSES OF OSCILLATOR FREQUENCY VARIATION   | 955 |
| (i) General                                   | 955 |
| (ii) Changes due to supply voltage            | 955 |
| (iii) Temperature and humidity changes        | 955 |
| (iv) Oscillator harmonics                     | 956 |
| 5. METHODS OF FREQUENCY STABILIZATION         | 957 |
| 6. UNSTABLE OSCILLATION                       | 958 |
| 7. PARASITIC OSCILLATION                      | 959 |
| 8. METHODS USED IN PRACTICAL DESIGN           | 959 |
| 9. BEAT FREQUENCY OSCILLATORS                 | 960 |
| 10. BIBLIOGRAPHY                              | 961 |

## CHAPTER 25. FREQUENCY CONVERSION AND TRACKING

|  |     |
|--|-----|
| 1. THE OPERATION OF FREQUENCY CONVERTERS AND MIXERS                                  | 962 |
| (i) Introduction   | 962 |
| (ii) General analysis of operation common to all types                               | 964 |
| (iii) The oscillator section of converter tubes                                      | 968 |
| (iv) The detailed operation of the modulator or mixer section of the converter stage | 968 |



## CONTENTS

| SECTION  | PAGE |
|--|------|
| (v) Conclusion   | 984  |
| (vi) Appendix  | 985  |
| 2. CONVERTER APPLICATIONS  | 987  |
| (i) Broadcast frequencies  | 987  |
| (ii) Short waves   | 990  |
| (iii) Types of converters  | 996  |
| 3. SUPERHETERODYNE TRACKING  | 1002 |
| (i) General  | 1002 |
| (ii) (A) Formulae and charts for superheterodyne oscillator design | 1005 |
| (B) Worked examples  | 1011 |
| (iii) (A) Padded signal circuits                                   | 1013 |
| (B) Worked example   | 1015 |
| 4. REFERENCES  | 1017 |

### CHAPTER 26. INTERMEDIATE FREQUENCY AMPLIFIERS

|  |      |
|--|------|
| 1. CHOICE OF FREQUENCY   | 1020 |
| (i) Reasons for selection of different frequencies             | 1020 |
| (ii) Commonly accepted intermediate frequencies                | 1021 |
| 2. NUMBER OF STAGES  | 1021 |
| 3. COMMONLY USED CIRCUITS                                      | 1022 |
| (i) Mutual inductance coupling                                 | 1023 |
| (ii) Shunt capacitance coupling                                | 1023 |
| (iii) Composite i-f transformers                               | 1024 |
| 4. DESIGN METHODS  | 1025 |
| (i) General  | 1025 |
| (ii) Critically-coupled transformers                           | 1026 |
| (A) Design equations and table                                 | 1026 |
| (B) Example  | 1028 |
| (C) Design extension   | 1029 |
| (D) Conclusions  | 1030 |
| (E) k measurement  | 1030 |
| (iii) Over-coupled transformers                                | 1031 |
| (A) Design equations and table                                 | 1031 |
| (B) Example  | 1033 |
| (C) k measurement (when k is high)                             | 1033 |
| (iv) Under-coupled transformers and single tuned circuits      | 1034 |
| (A) Single tuned circuit equations                             | 1034 |
| (B) Example  | 1035 |
| (C) Under-coupled transformer equations                        | 1035 |
| (D) Example  | 1036 |
| (v) F-M i-f transformers                                       | 1037 |
| (vi) I-F transformer construction                              | 1041 |
| (vii) Appendix: Calculation of coupling co-efficients          | 1043 |
| 5. VARIABLE SELECTIVITY  | 1048 |
| (i) General considerations                                     | 1048 |
| (ii) Automatic variable selectivity                            | 1049 |
| 6. VARIABLE BANDWIDTH CRYSTAL FILTERS                          | 1050 |
| (i) Behaviour of equivalent circuit                            | 1050 |
| (ii) Variable bandwidth crystal filters                        | 1052 |
| (iii) Design of variable bandwidth i-f crystal filter circuits | 1053 |
| (A) Simplifying assumptions                                    | 1053 |
| (B) Gain   | 1053 |
| (C) Gain variation with bandwidth change                       | 1054 |
| (D) Selectivity  | 1055 |

| SECTION | CONTENTS                             | PAGE |
|---------|--------------------------------------|------|
|         | (E) Crystal constants                | 1056 |
|         | (F) Position of filter in circuit    | 1057 |
|         | (G) Other types of crystal filters   | 1057 |
|         | (iv) Design example                  | 1057 |
| 7.      | DETUNING DUE TO A.V.C.               | 1061 |
|         | (i) Causes of detuning               | 1061 |
|         | (ii) Reduction of detuning effects   | 1062 |
| 8.      | STABILITY                            | 1065 |
|         | (i) Design data                      | 1065 |
|         | (ii) Neutralizing circuits           | 1065 |
| 9.      | DISTORTION                           | 1067 |
|         | (i) Amplitude modulation i-f stages  | 1067 |
|         | (ii) Frequency modulation i-f stages | 1068 |
| 10.     | REFERENCES                           | 1069 |

### CHAPTER 27. DETECTION AND AUTOMATIC VOLUME CONTROL

|    |                                       |      |
|----|---------------------------------------|------|
| 1. | A-M DETECTORS                         | 1072 |
|    | (i) Diodes                            | 1072 |
|    | (A) General                           | 1072 |
|    | (B) Diode curves                      | 1075 |
|    | (C) Quantitative design data          | 1075 |
|    | (D) Miscellaneous data                | 1081 |
|    | (ii) Other forms of detectors         | 1082 |
|    | (A) Grid detection                    | 1082 |
|    | (B) Power grid detection              | 1084 |
|    | (C) Plate detection                   | 1084 |
|    | (D) Reflex detection                  | 1085 |
|    | (E) Regenerative detectors            | 1086 |
|    | (F) Superregenerative detectors       | 1087 |
| 2. | F-M DETECTORS                         | 1088 |
|    | (i) Types of detectors in general use | 1088 |
|    | (ii) General principles               | 1088 |
|    | (iii) Phase discriminators            | 1088 |
|    | (A) General                           | 1088 |
|    | (B) Design data                       | 1090 |
|    | (C) Design example                    | 1091 |
|    | (iv) Ratio detectors                  | 1095 |
|    | (A) General                           | 1095 |
|    | (B) Operation                         | 1097 |
|    | (C) Types of circuit                  | 1098 |
|    | (D) Design considerations             | 1099 |
|    | (E) Practical circuits                | 1101 |
|    | (F) Measurement on ratio detectors    | 1102 |
| 3. | AUTOMATIC VOLUME CONTROL              | 1105 |
|    | (i) Introduction                      | 1105 |
|    | (ii) Simple a.v.c.                    | 1105 |
|    | (iii) Delayed a.v.c.                  | 1106 |
|    | (iv) Methods of feed                  | 1109 |
|    | (v) Typical circuits                  | 1111 |
|    | (vi) A.V.C. application               | 1111 |
|    | (vii) Amplified a.v.c.                | 1112 |
|    | (viii) Audio a.v.c.                   | 1113 |
|    | (ix) Modulation rise                  | 1114 |

## CONTENTS

| SECTION  | PAGE |
|--|------|
| (x) A.V.C. with battery valves                     | 1114 |
| (xi) Special case with simple a.v.c.               | 1115 |
| (xii) The a.v.c. filter and its time constants     | 1115 |
| (xiii) A.V.C. characteristics                      | 1117 |
| (xiv) An improved form of a.v.c. characteristic    | 1118 |
| (xv) Design methods                                | 1120 |
| 4. MUTING (Q.A.V.C.)                               | 1125 |
| (i) General operation                              | 1125 |
| (ii) Typical circuits                              | 1125 |
| (iii) Circuits used with F-M receivers             | 1128 |
| 5. NOISE LIMITING                                  | 1130 |
| 6. TUNING INDICATORS                               | 1132 |
| (i) Miscellaneous                                  | 1132 |
| (ii) Electron Ray tuning indicators                | 1133 |
| (iii) Null point indicator using Electron Ray tube | 1134 |
| (iv) Indicators for F-M receivers                  | 1135 |
| 7. CRYSTAL DETECTORS                               | 1136 |
| (i) Old type crystal detectors                     | 1136 |
| (ii) Fixed germanium crystal detectors             | 1136 |
| (iii) Fixed silicon crystal detectors              | 1137 |
| (iv) Theory of crystal rectification               | 1138 |
| (v) Transistors                                    | 1138 |
| 8. REFERENCES                                      | 1138 |

### CHAPTER 28. REFLEX AMPLIFIERS

|  |      |
|--|------|
| 1. GENERAL DESCRIPTION   | 1140 |
| (i) Description  | 1140 |
| (ii) Advantages and disadvantages of reflex receivers            | 1140 |
| 2. SOME CHARACTERISTICS OF REFLEX SUPERHET. RECEIVERS            | 1142 |
| (i) Playthrough (residual volume effect)                         | 1142 |
| (ii) Over-loading  | 1142 |
| (iii) Automatic volume control                                   | 1142 |
| (iv) Reduction in percentage modulation                          | 1143 |
| (v) Negative feedback  | 1143 |
| (vi) Operating conditions of reflex stage                        | 1143 |
| 3. DESIGN OF PLATE REFLEX SUPERHET. RECEIVERS                    | 1143 |
| (i) General considerations                                       | 1143 |
| (ii) Full a.v.c. applied to both stages                          | 1143 |
| (iii) Fractional a.v.c. applied to both stages                   | 1143 |
| (iv) Full a.v.c. on converter, fractional a.v.c. on reflex stage | 1144 |
| 4. DESIGN OF SCREEN REFLEX SUPERHET. RECEIVERS                   | 1145 |
| (i) Screen reflex receivers                                      | 1145 |
| (ii) Comparison between plate and screen reflexing               | 1146 |
| 5. DESIGN OF T.R.F. REFLEX RECEIVERS                             | 1146 |
| 6. REFERENCES TO REFLEX AMPLIFIERS AND REFLEX RECEIVERS          | 1146 |

### CHAPTER 29. LIMITERS AND AUTOMATIC FREQUENCY CONTROL

|   |      |
|---|------|
| 1. LIMITERS                             | 1147 |
| (i) General                             | 1147 |
| (ii) Typical circuits for F-M receivers | 1149 |
| 2. AUTOMATIC FREQUENCY CONTROL          | 1150 |
| (i) General principles                  | 1150 |
| (ii) Discriminators for a.f.c.          | 1152 |
| (iii) Electronic reactances             | 1156 |
| 3. REFERENCES                           | 1160 |

## CONTENTS

| SECTION |   | PAGE |
|---------|---|------|
|         | <b>PART 5: RECTIFICATION, REGULATION, FILTERING AND HUM</b>   |      |
|         | <b>CHAPTER 30. RECTIFICATION</b>                              |      |
| 1.      | INTRODUCTION TO RECTIFICATION                                 | 1161 |
|         | (i) Principles of rectification                               | 1161 |
|         | (ii) Rectifier valves and types of service                    | 1164 |
|         | (iii) The use of published curves                             | 1165 |
|         | (iv) Selenium and copper oxide rectifiers                     | 1169 |
| 2.      | RECTIFICATION WITH CONDENSER INPUT FILTER                     | 1170 |
|         | (i) Symbols and definitions                                   | 1170 |
|         | (ii) Rectification with condenser input filter                | 1170 |
|         | (iii) To determine peak and average diode currents            | 1174 |
|         | (iv) To determine ripple percentage                           | 1177 |
|         | (v) To determine the transformer secondary r.m.s. current     | 1177 |
|         | (vi) Procedure when complete published data are not available | 1177 |
|         | (vii) Approximations when the capacitance is large            | 1180 |
|         | (viii) Peak hot-switching transient plate current             | 1180 |
|         | (ix) The effect of ripple                                     | 1181 |
| 3.      | RECTIFICATION WITH CHOKE INPUT FILTER                         | 1182 |
|         | (i) Rectification with choke input filter                     | 1182 |
|         | (ii) Initial transient current                                | 1185 |
| 4.      | TRANSFORMER HEATING   | 1185 |
| 5.      | VOLTAGE MULTIPLYING RECTIFIERS                                | 1186 |
|         | (i) General   | 1186 |
|         | (ii) Voltage doublers   | 1186 |
|         | (iii) Voltage triplers  | 1187 |
|         | (iv) Voltage quadruplers                                      | 1187 |
| 6.      | SHUNT DIODE BIAS SUPPLIES                                     | 1188 |
|         | <b>CHAPTER 31. FILTERING AND HUM</b>                          |      |
| 1.      | INDUCTANCE-CAPACITANCE FILTERS                                | 1192 |
| 2.      | RESISTANCE-CAPACITANCE FILTERS                                | 1194 |
| 3.      | PARALLEL-T FILTER NETWORKS                                    | 1194 |
| 4.      | HUM—GENERAL   | 1196 |
|         | (i) Hum due to conditions within the valves                   | 1196 |
|         | (ii) Hum due to circuit design and layout                     | 1198 |
|         | (iii) Hum levels in receivers and amplifiers                  | 1199 |
| 5.      | HUM NEUTRALIZING  | 1200 |
| 6.      | REFERENCES  | 1201 |
|         | <b>CHAPTER 32. VIBRATOR POWER SUPPLIES</b>                    |      |
| 1.      | VIBRATORS—GENERAL PRINCIPLES                                  | 1202 |
|         | (i) Operation   | 1202 |
|         | (ii) Vibrator types   | 1202 |
|         | (iii) Choice of vibrator                                      | 1203 |
|         | (iv) Coil energizing  | 1204 |
|         | (v) Waveform and time efficiency                              | 1205 |
|         | (vi) Standards for vibrators for auto-radio                   | 1205 |

## CONTENTS

| SECTION   | PAGE |
|---|------|
| 2. VIBRATOR TRANSFORMER DESIGN                                | 1205 |
| (i) General considerations                                    | 1205 |
| (ii) Transformer calculations                                 | 1206 |
| (iii) Standards for vibrator power transformers               | 1207 |
| 3. TIMING CAPACITANCE   | 1207 |
| (i) The use of the timing capacitance                         | 1207 |
| (ii) Calculation of timing capacitance value                  | 1207 |
| (iii) Percentage closure                                      | 1208 |
| (iv) Effect of flux density on timing capacitance value       | 1208 |
| 4. ELIMINATION OF VIBRATOR INTERFERENCE                       | 1210 |
| 5. 12, 24 AND 32 VOLT VIBRATOR SUPPLIES                       | 1211 |
| <b>CHAPTER 33. CURRENT AND VOLTAGE REGULATORS</b>             |      |
| 1. CURRENT REGULATORS   | 1213 |
| (i) Barretters  | 1213 |
| (ii) Negative temperature coefficient resistors (Thermistors) | 1214 |
| 2. VOLTAGE REGULATORS   | 1214 |
| (i) Gaseous tube voltage regulators                           | 1214 |
| (ii) Valve voltage regulators                                 | 1215 |
| 3. REFERENCES   | 1222 |
| <b>PART 6: COMPLETE RECEIVERS</b>                             |      |
| <b>CHAPTER 34. TYPES OF A-M RECEIVERS</b>                     |      |
| 1. INTRODUCTION AND SIMPLE RECEIVERS                          | 1223 |
| (i) Types of receivers  | 1223 |
| (ii) Crystal sets   | 1223 |
| (iii) Regenerative receivers                                  | 1223 |
| (iv) Superheterodyne receivers                                | 1224 |
| (v) Tuned radio-frequency receivers                           | 1224 |
| 2. THE SUPERHETERODYNE  | 1225 |
| 3. THE SYNCHRODYNE  | 1226 |
| 4. REFERENCES   | 1227 |
| <b>CHAPTER 35. DESIGN OF SUPERHETERODYNE A-M RECEIVERS</b>    |      |
| 1. INTRODUCTION   | 1228 |
| 2. SPECIFICATIONS AND REQUIREMENTS                            | 1229 |
| 3. GENERAL DESIGN   | 1229 |
| (i) A.V.C. and noise  | 1229 |
| (ii) Audio-frequency response                                 | 1234 |
| (iii) Hum   | 1239 |
| (iv) Microphony   | 1241 |
| (v) Instability   | 1243 |
| (vi) The local oscillator                                     | 1244 |
| (vii) Cabinet design  | 1248 |
| (viii) Ratings  | 1249 |
| (ix) Field testing  | 1250 |
| 4. FREQUENCY RANGES   | 1250 |
| (i) Medium frequency receivers                                | 1250 |
| (ii) Dual wave receivers                                      | 1251 |
| (iii) Multiband receivers                                     | 1252 |
| (iv) Bandsread receivers                                      | 1253 |

## CONTENTS

| SECTION                                | PAGE |
|--|------|
| 5. A.C. OPERATED RECEIVERS             | 1256 |
| (i) Four valve receivers               | 1256 |
| (ii) Five valve receivers              | 1259 |
| (iii) Larger receivers                 | 1260 |
| (iv) Communication receivers           | 1260 |
| 6. A.C./D.C. RECEIVERS                 | 1264 |
| (i) Series-resistor operation          | 1264 |
| (ii) Barretter operation               | 1266 |
| (iii) Dial lamps                       | 1266 |
| (iv) Miscellaneous features            | 1267 |
| 7. BATTERY OPERATED RECEIVERS          | 1268 |
| (i) General features                   | 1268 |
| (ii) Vibrator-operated receivers       | 1270 |
| (iii) Characteristics of dry batteries | 1272 |
| 8. CAR RADIO                           | 1275 |
| (i) Interference suppression           | 1275 |
| (ii) Circuit considerations            | 1276 |
| (iii) Valve operating conditions       | 1277 |
| 9. MISCELLANEOUS FEATURES              | 1278 |
| (i) Spurious responses                 | 1278 |
| (ii) Reduction of interference         | 1279 |
| (iii) Contact potential biasing        | 1280 |
| (iv) Fuses                             | 1281 |
| (v) Tropic proofing                    | 1282 |
| (vi) Parasitic oscillations            | 1283 |
| (vii) Printed circuits                 | 1283 |
| (viii) Other miscellaneous features    | 1285 |
| 10. REFERENCES                         | 1285 |

### CHAPTER 36. DESIGN OF F-M RECEIVERS

|                                     |      |
|-------------------------------------|------|
| 1. F-M RECEIVERS                    | 1287 |
| (i) Comparison with A-M             | 1287 |
| (ii) Aerial and r-f design          | 1287 |
| (iii) Local oscillator design       | 1289 |
| (iv) I-F amplifier                  | 1290 |
| (v) F-M detection and A-M rejection | 1292 |
| 2. F-M/A-M RECEIVERS                | 1294 |
| (i) R-F section                     | 1294 |
| (ii) I-F amplifier                  | 1294 |
| (iii) General considerations        | 1295 |
| 3. REFERENCES                       | 1296 |

### CHAPTER 37. RECEIVER AND AMPLIFIER TESTS AND MEASUREMENTS

|  |      |
|--|------|
| 1. A-M RECEIVERS                           | 1297 |
| (i) Introduction                           | 1297 |
| (ii) Definitions                           | 1297 |
| (iii) Equipment required                   | 1298 |
| (iv) Measurements and operating conditions | 1300 |
| (v) Measurements                           | 1301 |
| (vi) Tests                                 | 1302 |
| 2. F-M RECEIVERS                           | 1314 |
| (i) Definitions                            | 1314 |
| (ii) Testing apparatus                     | 1315 |

## CONTENTS

| SECTION  | PAGE |
|--|------|
| (iii) Test procedures and operating conditions                           | 1315 |
| (iv) Receiver adjustments  | 1316 |
| (v) Performance tests  | 1317 |
| 3. AUDIO FREQUENCY AMPLIFIERS  | 1321 |
| (i) Equipment and measurements   | 1321 |
| (ii) Tests   | 1321 |
| 4. MEASUREMENTS ON COILS   | 1325 |
| (i) Measurement of coefficient of coupling                               | 1325 |
| (ii) Measurement of primary resonant frequencies of aerial and r-f coils | 1325 |
| (iii) Measurement of distributed capacitance across coils                | 1325 |
| 5. REFERENCES  | 1327 |

## PART 7: SUNDRY DATA

### CHAPTER 38. TABLES, CHARTS AND SUNDRY DATA

|   |      |
|---|------|
| 1. UNITS  | 1329 |
| (i) General physical units  | 1329 |
| (ii) Electrical and magnetic units  | 1331 |
| (iii) Photometric units   | 1334 |
| (iv) Temperature  | 1334 |
| 2. COLOUR CODES   | 1335 |
| (i) Colour code for fixed composition resistors                           | 1335 |
| (ii) Colour code for fixed wire wound resistors                           | 1336 |
| (iii) Table of R.M.A. colour code markings for resistors                  | 1337 |
| (iv) Colour code for moulded mica capacitors                              | 1340 |
| (v) Colour code for ceramic dielectric capacitors                         | 1341 |
| (vi) Colour code for i-f transformers                                     | 1342 |
| (vii) Colour code for a-f transformers and output transformers            | 1342 |
| (viii) Colour code for power transformers                                 | 1342 |
| (ix) Colour code for loudspeakers   | 1343 |
| (x) Colour code for chassis wiring  | 1343 |
| (xi) Colour code for battery cables                                       | 1344 |
| (xii) Colour code for metallized paper capacitors                         | 1344 |
| 3. STANDARD RESISTORS AND CAPACITORS                                      | 1344 |
| (i) Standard fixed composition resistors                                  | 1344 |
| (ii) Standard fixed wire wound resistors                                  | 1346 |
| (iii) Fixed paper dielectric capacitors in tubular non-metallic cases     | 1347 |
| (iv) Metal encased fixed paper dielectric capacitors for d.c. application | 1349 |
| (v) Standard fixed mica dielectric capacitors                             | 1351 |
| (vi) Standard ceramic dielectric capacitors                               | 1352 |
| (vii) Standard variable capacitors  | 1354 |
| (viii) Standard variable composition resistors                            | 1356 |
| (ix) Standard metallized paper dielectric capacitors                      | 1357 |
| (x) Standard electrolytic capacitors                                      | 1357 |
| (xi) References to standard resistors and capacitors                      | 1358 |
| 4. STANDARD FREQUENCIES   | 1361 |
| (i) Standard frequency ranges   | 1361 |
| (ii) Frequency bands for broadcasting                                     | 1361 |
| (iii) Standard intermediate frequencies                                   | 1361 |
| 5. WAVELENGTHS AND FREQUENCIES  | 1362 |
| (i) Wavelength-frequency conversion tables                                | 1362 |
| (ii) Wavelengths of electromagnetic radiations                            | 1363 |
| 6. STANDARD SYMBOLS AND ABBREVIATIONS                                     | 1363 |
| (i) Introduction  | 1363 |
| (ii) Multipliers 1363   | 1363 |

## CONTENTS

| SECTION   | PAGE |
|---|------|
| (iii) Some units and multipliers  | 1363 |
| (iv) Magnitude letter symbols   | 1364 |
| (v) Subscripts for magnitude letter symbols   | 1364 |
| (vi) Magnitude letter symbols with subscripts   | 1365 |
| (vii) Mathematical signs  | 1366 |
| (viii) Abbreviations  | 1366 |
| (ix) Abbreviations of titles of periodicals   | 1367 |
| (x) References to periodicals   | 1369 |
| (xi) References to standard symbols and abbreviations   | 1369 |
| 7. STANDARD GRAPHICAL SYMBOLS   | 1370 |
| 8. PROPERTIES OF MATERIALS AND CHEMICAL AND PHYSICAL CONSTANTS  | 1372 |
| (i) Properties of insulating materials  | 1372 |
| (ii) Properties of conducting materials   | 1374 |
| (iii) Composition of some common plastics   | 1375 |
| (iv) Weights of common materials  | 1375 |
| (v) Resistance of a conductor at any temperature  | 1376 |
| (vi) References to properties of materials  | 1376 |
| (vii) Chemical and physical constants   | 1376 |
| 9. REACTANCE, IMPEDANCE AND RESONANCE   | 1377 |
| (i) Inductive reactances  | 1377 |
| (ii) Capacitive reactances  | 1378 |
| (iii) Impedance of reactance and resistance in parallel   | 1380 |
| (iv) Impedance of reactance and resistance in series  | 1382 |
| (v) Resonance   | 1386 |
| (vi) Approximations in the calculation of impedance for reactance<br>and resistance in series and parallel  | 1386 |
| (vii) Reactance chart   | 1387 |
| 10. SCREW THREADS, TWIST DRILLS AND SHEET GAUGES  | 1388 |
| (i) Standard American screws used in radio manufacture  | 1388 |
| (ii) B.A. screw threads   | 1389 |
| (iii) Whitworth screw threads   | 1389 |
| (iv) Unified screw threads  | 1390 |
| (v) Drill sizes for self-tapping screws   | 1391 |
| (vi) Wood screws  | 1391 |
| (vii) Twist drill sizes   | 1392 |
| (viii) Sheet steel gauges   | 1393 |
| 11. TEMPERATURE RISE AND RATINGS  | 1394 |
| 12. FUSES   | 1395 |
| 13. CHARACTERISTICS OF LIGHT; PANEL LAMPS   | 1396 |
| (i) Visibility curves of the human eye and relative spectral energy<br>curves of sunlight and tungsten lamp | 1396 |
| (ii) Velocity of light  | 1396 |
| (iii) American panel lamp characteristics   | 1397 |
| 14. GREEK ALPHABET  | 1397 |
| 15. DEFINITIONS   | 1398 |
| 16. DECIMAL EQUIVALENTS OF FRACTIONS  | 1404 |
| 17. MULTIPLES AND SUB-MULTIPLES   | 1405 |
| 18. (i) Numerical values  | 1406 |
| (ii) Factorials   | 1407 |
| 19. WIRE TABLES   | 1408 |
| 20. LOGARITHM TABLES  | 1418 |
| 21. TRIGONOMETRICAL TABLES  | 1420 |
| Hyperbolic sines, cosines and tangents  | 1421 |
| 22. LOG SCALES AND LOG SCALE INTERPOLATOR   | 1422 |